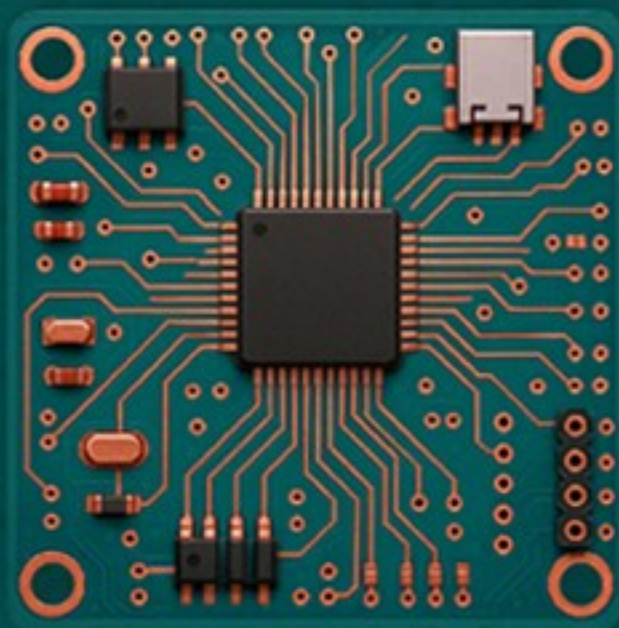


DESIGN REVIEW CHECKLIST

Schematic Circuit



- ✓ Ensure that there are no missing net ties and schematic ports across all schematic sheets.
- ✓ Ensure that design rules matching the PCB manufacturer's capabilities have been implemented.
- ✓ Ensure that all component decoupling capacitors be clearly identified, with a proper note about placement close to the supply pins of the processor.
- ✓ Add appropriate notes regarding:
 - a trace width for high current traces
 - b trace length matching for high-speed traces with matching propagation delay requirements.
 - c controlled impedance traces, include the expected impedance of such traces.
 - d traces carrying low noise signals. Indicate that they are to be separated from high current traces or traces carrying fast signals.
 - e trace separation clearances for high voltage trace. Indicate if physical barriers such as PCB slots are needed.
- ✓ Properly identify passive components with specific characteristics such as high power or precision resistors, low temperature coefficient, or low ESR capacitors and others
- ✓ Unused pins on IC's should be confirmed to be no net connection, or pulled up or pulled down.
- ✓ Check all schematic capture compilation warnings. Do not ignore any unless there is a good reason for doing so.
- ✓ Ensure the IC outputs such as I2C SDA or SCL have proper pull-up resistors.

- ✓ Ensure the IC outputs such as I2C SDA or SCL have proper pull-up resistors.
- ✓ Ensure that clamp diodes and transient suppressors have been included in all externally exposed connections.
- ✓ If there are different types of Ground, eg. Signal ground or Power ground, make sure to properly label each ground with its type.
- ✓ Identify magnetic components, such as power inductors, that could cross-couple. Make a note about properly spacing, or orienting, them.
- ✓ Identify high heat generating components and temperature sensitive components, and add a note that they are to be properly physically separated.
- ✓ Identify circuit sections that need to be shielded, and indicate the type of shielding, such as cans, needed.
- ✓ Indicate the need of guard rings around very sensitive low-level signal input pins.
- ✓ Do not place high voltage and low voltage lines adjacent to each other on connector pins on the schematic.
- ✓ Use multiple connector pins for carrying high current, taking into account the current carrying capability of each pin of the selected connector.
- ✓ If using PCB heatsink or on-board heatsinks, specify keep-out area.
- ✓ Specify Do-Not-Populate (DNP) components.
- ✓ Add appropriate test points to critical nodes.
- ✓ Specify test point surface treatment, if required.
- ✓ Specify surface treatment, such as gold plating of a given thickness, for

- ✓ Sufficient clearances between high voltage traces.
- ✓ Trace widths are sufficient for traces carrying large currents.
- ✓ Low noise traces do not run too close to high-current traces or high-speed digital traces.
- ✓ For high-speed traces, ensure that line lengths are properly matched. The higher end layout packages have tools to do this.
- ✓ For high-speed traces also run simulations to ensure that there are no violations, including the effects of vias on signal propagation.
- ✓ Consider the effect of ground loops for designs without a proper ground plane.
- ✓ Be aware of the placement and orientation of magnetic components, if any, to avoid cross coupling.
- ✓ For very low-level signals, make sure that the appropriate guard rings are in place.
- ✓ Depending on the frequency of the signal, the typical FR4 substrate may not be suitable, and a low loss, but more expensive, substrate should be considered.
- ✓ Ensure that any RF lines have the proper complex impedance (typically 50 ohms). This includes confirming that a ground layer is underneath the trace (microstrip) and commonly on both sides as well (coplanar waveguide).
- ✓ On-board antennas have the proper ground clearances on all layers.
- ✓ Ground layers have sufficient stitching vias especially near any RF circuits.
- ✓ On-board chip antennas are placed according to the manufacturer's recommendations.

- ✓ If the design includes multiple on-board antennas be sure they are placed so as to maximize their distance to prevent cross interference.
- ✓ Switching power regulators are carefully laid out according to the manufacturer's datasheet.
- ✓ Power supply pins on any IC's have decoupling capacitors placed nearby.
- ✓ No footprint errors it's best to print out the layout at scale, and then physically lay all of the components on the printout to ensure the leads match up properly.
- ✓ Test points are included on all signal traces which aren't easily accessed (i.e. signals between leadless packages).
- ✓ No blind or buried vias are used unless absolutely required. Their use will significantly increase the board cost.
- ✓ Final board dimensions match correctly with the enclosure design.
- ✓ Any crystal connections are kept as short as possible.
- ✓ All components, connectors, jumpers, and test points are properly labeled in the silkscreen layer.
- ✓ No signal traces have 90-degree bends
- ✓ Signal traces don't unnecessarily jump between different board layers. This can also be a sign of auto-routing, which rarely produces a quality design.
- High-current traces are primarily routed on the outside layers.
- ✓ Silkscreen layer includes the proper board part number and the current revision.

- ✓ If required for assembly, confirm that the design includes the necessary fiducial.
- ✓ Polarities are marked for polarized components like some capacitors.
- ✓ Pin 1 is marked on all integrated circuits.
- ✓ Digital and analog sections are kept separated with grounds connected at a single point.
- ✓ Generate a 3D model of the PCB, and make sure that there is no interference with other parts of the device assembly.
- ✓ Design rules match the capabilities of the specific PCB manufacturer.

For Entrepreneurs and Startups:

Develop and launch your electronic product **FASTER** without costly mistakes!

Doing it alone is slow and risky. Small missteps now can become big problems later. Skip the mistakes and launch faster.

→ Frustrated things aren't moving as fast as you want?

Feeling unsure what to do next? ←

Meet your guide: John Teel



Hey there, I'm a former microchip design engineer at Texas Instruments and founder of a hardware startup that sold products in hundreds of retail stores. My chip designs are in devices from Apple, Intel, and more.

Now, my full-time focus is helping people like you bring new electronic products to life, without wasting time, money, or risking everything.

**CLICK HERE
TO LEARN MORE!**